



5-8 System Design Applications

Let's summarize the entire chapter now by working through two complete design problems. The following examples illustrate practical applications of a K-map to ensure that when we implement the circuit using an AOI, we will have the simplest possible solution.

NOTE: The construction of digital circuits with higher complexity than those of these examples will be more practically suited for implementation using PLDs, which are discussed in Section 5-9.

SYSTEM DESIGN 5-1

Design a circuit that can be built using an AOI and inverters that will output a HIGH (1) whenever the 4-bit hexadecimal input is an odd number from 0 to 9.

Table 5-7 Hex Truth Table Used to Determine the Equation for Odd Numbers from 0 to 9

D	C	B	A	DEC
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

$$\text{Odd number} = \overline{A}BCD + A\overline{B}CD + AB\overline{C}D + ABC\overline{D} + \overline{A}BC\overline{D} + A\overline{B}C\overline{D} + AB\overline{C}\overline{D} + ABC\overline{D}$$

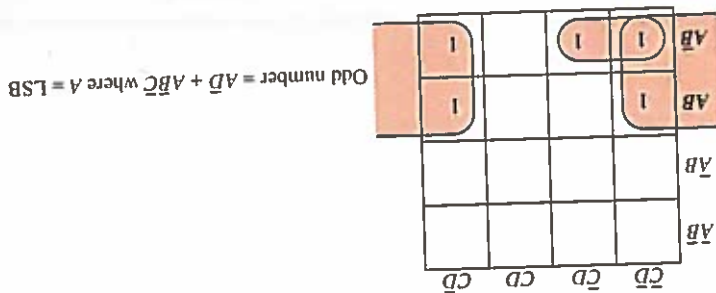


Figure 5-76 (a) Simplified equation derived from a Karnaugh map;

The LSB (variable A) is always HIGH for an odd number. Why can't we just say "odd number = A"?

