

Also, all four corners are adjacent to each other because the K-map can be wrapped around in both the vertical *and* horizontal directions. Encircling the four corners results in $\overline{B}D$. The final equation is

$$X = \overline{A} + \overline{B}D$$

EXAMPLE 3-20

Simplify the following equation using the Karnaugh mapping procedure:

$$X = \overline{A}\overline{B}\overline{D} + A\overline{C}\overline{D} + \overline{A}B\overline{C} + AB\overline{C}D + A\overline{B}C\overline{D}$$

Solution:

Encircling the four corners forms $\overline{B}D$, as shown in Figure 3-45. The other group of four forms $B\overline{C}$. You may be tempted to encircle the $\overline{C}\overline{D}$ group of four as shown by the dotted line, but that would be *redundant* because each of those 1s is already contained within an existing circle. Therefore, the final equation is

$$X = \overline{B}D + B\overline{C}$$

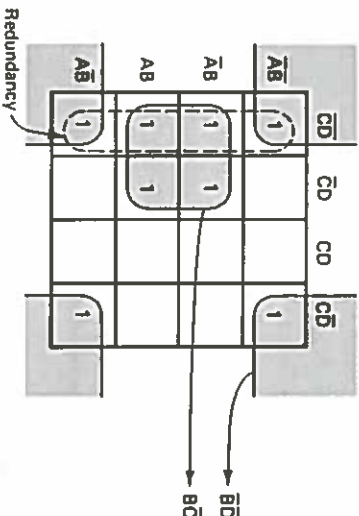


Figure 3-45 Solution to Example 3-20.

3-6 SYSTEM DESIGN APPLICATIONS

Let's summarize the entire chapter now by working through two complete design problems. The following examples illustrate practical applications of a K-map to ensure that when we implement the circuit we will have the simplest possible solution.

Note: The construction of digital circuits with higher complexity than those of these examples will be more practically suited for implementation using what is called *programmable logic devices*, which are discussed in Chapter 8 and Appendix K.

SYSTEM DESIGN 3-1

Design a circuit that can be built using logic gates that will output a HIGH (1) whenever the 4-bit BCD input is an odd number from 0 to 9.


Solution:

First, build a truth table (Table 3-3) to identify which BCD codes from 0 to 9 produce odd numbers. (Use the variable A to represent the 2^0 BCD input, B for 2^1 , C for 2^2 , and D for 2^3 .) Next, reduce that equation into its simplest form by using a Karnaugh map, as shown in Figure 3-46a. Finally, using basic logic gates, the circuit can be constructed, as shown in Figure 3-46b.

TABLE 3-3
Truth Table Used to Determine the Equation for Odd Numbers* from 0 to 9

D	C	B	A	DEC
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9

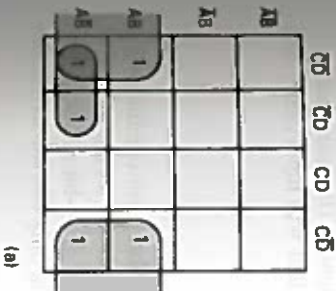*Odd number = $A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D} + A\overline{B}C\overline{D} + A\overline{B}C\overline{D} + A\overline{B}C\overline{D} + A\overline{B}C\overline{D} + A\overline{B}C\overline{D} + A\overline{B}C\overline{D}$



Odd number = $A\overline{D} + A\overline{B}\overline{C}$ where A = LSB

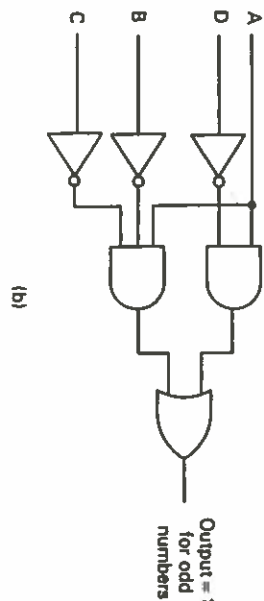


Figure 3-46 (a) Simplified equation derived from a Karnaugh map; (b) logic circuit for the "odd-number decoder."

SYSTEM DESIGN 3-2

A chemical plant needs an alarm system developed to warn of critical conditions in one of its chemical tanks. The tank has four HIGH/LOW (1/0) switches, monitoring temperature (T), pressure (P), fluid level (L), and weight (W). Design a system that will activate an alarm when any of the following conditions arise:

1. A high fluid level with a high temperature and a high pressure
2. A low fluid level with a high temperature and a high weight
3. A low fluid level with a low temperature and a high pressure
4. A low fluid level with a low weight and a high temperature

Solution:

First, write in Boolean equation form, the conditions that will activate the alarm:

$$\text{Alarm} = LTP + \overline{L}TW + \overline{L}\overline{T}P + \overline{L}\overline{W}T$$

Next, factor the equation into its simplest form by using a Karnaugh map, as shown in Figure 3-47a. Finally, the logic circuit can be constructed, as shown in Figure 3-47b.