

Contents

2.4.2	Equality of Expressions	59
2.4.3	Duality	59
2.5	Functions and Their Representations	59
2.5.1	Truth Tables	60
2.5.2	Venn Diagrams	61
2.5.3	Algebraic Representations	63
2.6	Theorems	69
2.6.1	Expansion to Canonical Forms	75
2.6.2	Proving the Equality of Expressions	77
2.6.3	Simplifying Boolean Functions	78
2.7	Other Operations	80
2.7.1	A Functionally Complete Set of Operators	82
2.8	Multiple-Input Gates and Logic Circuits	83
2.9	Integrated Circuits	86
2.9.1	Positive and Negative Logic	90
2.9.2	Signal Inversion	92
2.9.3	Noise Margin	93
2.9.4	Loading and Fan-out	96
2.9.5	Speed and Power Dissipation	97
2.10	Summary	97
	References	98
	Problems	98

3 Minimization of Boolean Functions 102

3.1	K-maps	103
3.1.1	Representation of Functions on K-maps	106
3.1.2	Plotting the SOP Form	108
3.1.3	Plotting the POS Form	110
3.1.4	Minimization	111
3.2	Incompletely Specified Functions	118
3.3	Quine-McCluskey Procedure	122
3.3.1	Covering Problem	128
3.3.2	Multiple-Output Functions	132
3.4	Summary	134
	References	134
	Problems	135

4 Combinational Circuits 137

4.1	Introduction	137
4.2	Functional Analysis	138
4.3	Design	140
4.3.1	AND-OR Circuits	142
4.3.2	OR-AND Circuits	143

4.3.3	NAND-NAND Circuits	144
4.3.4	NOR-NOR Circuits	144
4.4	Other Two-Level Circuits	155
4.5	EXCLUSIVE-OR and EQUIVALENCE	157
4.6	Multiple-Level Circuits Revisited	162
4.7	Timing Analysis	165
4.7.1	Hazards	168
4.8	Loading Analysis	170
4.9	Designing with ICs	171
4.10	Special ICs	173
4.10.1	Buffers	173
4.10.2	Special Outputs	173
4.11	Summary	179
	References	179
	Problems	179

5 Integrated Circuits 183

5.1	Introduction	183
5.2	IC Fabrication	184
*5.3	Bipolar IC Technologies	186
5.3.1	Diode Logic Gates	187
5.3.2	Transistor Logic Gates	190
5.3.3	RTL Gates	195
5.3.4	DTL Gates	196
5.3.5	TTL Logic	197
5.3.6	ECL Gates	210
*5.4	Metal Oxide Semiconductor (MOS) IC Technology	214
5.4.1	NMOS Logic Gates	216
5.4.2	CMOS Logic	218
*5.5	Gallium Arsenide IC Technology	223
5.6	Summary	227
	References	227
	Problems	228

6 Popular Combinational Circuits 231

6.1	Introduction	231
6.2	Adders	233
6.2.1	Parallel Binary Adder (PBA)	233
6.2.2	Carry Lookahead Adder (CLA)	236
6.2.3	Off-the-Shelf Adders	238
6.2.4	Decimal Adder	246
6.3	Magnitude Comparators	249
6.4	Shifters	249